



NOTE: ALL CAPACITORS IN  $\mu$ F (MICROFARADS) UNLESS OTHERWISE NOTED.

Fig. 2-25. Schematic diagram of Novice-Class 60-watt station.

Pentode plate current is largely unaffected by changes in plate voltage contributing to the amplitude stability of the plate tank oscillation. R3 is a voltage divider for the screen grid feedback in a 3:2 ratio, Current flow to the screen is Plate voltage/33K